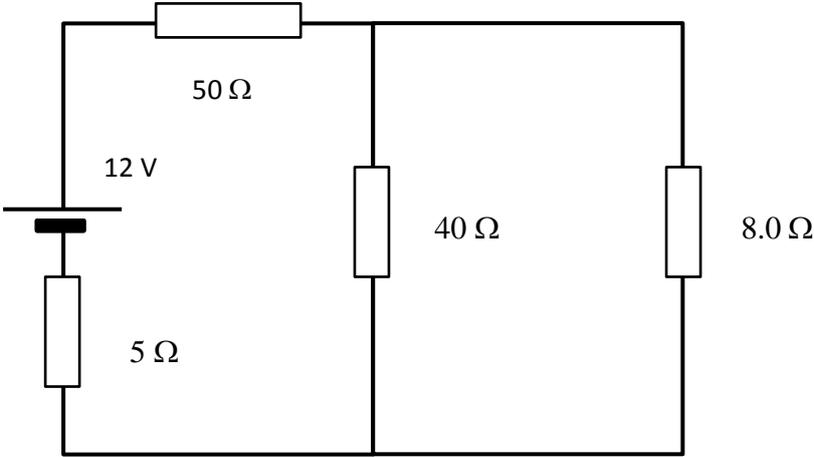



Answers to Semester 2 Examination on Electrical Principles

Examination Time – 120 minutes


- *Marking points are indicated by ticks (✓).*
- *Credit is awarded for each step.*
- *Credit may be awarded for correct or valid answers that are not on this marking scheme.*
- *A correct answer with no working gains the allotted mark minus one.*
- *Arithmetical errors are denoted with a.e.*
- *Physics errors are denoted with p.e and marking for that part ceases.*
- *All errors can be carried forward (e.c.f.).*
- *Where an error is carried forward, full credit can be awarded for the correct use of the error.*
- *Unit errors are penalised once only.*
- *Significant figure errors are penalised once only.*
- *Missing material is denoted by carets (^).*
- *Unattempted questions should be crossed out with a diagonal straight line.*

1.	Electrical engineers use the concepts of ideal constant voltage source and constant current sources to help them to analyse circuits		
(a)	State what is meant by: (i) A constant voltage source; (ii) A constant current source.	4.2	(4)
	(i) A constant voltage source can maintain a specific voltage...		✓
	...regardless of the current drawn.		✓
	(ii) Ideal constant current source gives out a specific current...		✓
	...regardless of the voltage.		✓
(b)	In reality circuits are not ideal. Leon Thévenin devised simple a rule that enabled electrical engineers to analyse circuits that did not have idea voltage sources. Write down Thévenin's Theorem.		(2)
	Any source however complex can be represented as...		✓
	...a simple perfect battery in series with an internal resistor.		✓
(c)	The diagram shows a circuit:  Show that the Thévenin Voltage is about 5 V		(4)
	(Remove the 8 Ω resistor)		
	Total resistance = 95 Ω		✓
	$I = 12 \div 95 = 0.126 \text{ A}$		✓
	$V_{Th} = 0.126 \times 40$		✓
	$V_{Th} = 5.1 \text{ V } (\approx 5 \text{ V})$		✓

(d)	Show that the Thévenin resistance is about 23Ω	(4)
	(Remove the battery and short out the gap, then peer in)	✓
	Work out the series resistors = $50 + 5 = 55 \Omega$	✓
	Work out the parallel resistors = $55^{-1} + 40^{-1} = 0.431$	✓
	$R_{Th} = 23.2 \Omega (\approx 23 \Omega)$	✓
(e)	Work out the current in the 8.0Ω resistor.	(3)
	$R + r = 23.2 + 8 = 31.2 \Omega$	✓
	$I = 5.1 \div 31.2$	✓
	$I = 0.16 \text{ A}$	✓
(f)	Work out the power dissipated in the 8.0 ohm resistor.	(3)
	$P = 0.163^2 \times 8$	✓
	$P = 0.21 \text{ W}$	✓
(g)	<p>A student says that the maximum useful power transfer occurs when the current is at a maximum (i.e. when the source is shorted out). Another student says that it occurs when the outside load resistance is the same as the Thévenin resistance. A third student suggests that the power transfer is much higher when the outside resistance is higher than the Thévenin resistance.</p> <p>Using $R = 0, 23 \Omega$ and 50Ω, demonstrate with suitable supporting calculations if necessary which student is correct.</p>	4.5 (7)
	At short circuit, the useful power transfer is zero.	✓
	When $R = r, V = 5.05 \div 2 = 2.53 \text{ V}$	✓
	$P = 2.525^2 \div 23.2 = 0.27 \text{ W}$	✓
	When $R > 23 \Omega, P$ is reduced.	✓
	$R = 50 \Omega$, therefore $R_T = 73.2 \Omega$	✓
	$V = (50/73.2) \times 5.05 = 3.45 \text{ V}$	✓
	$P = 3.45^2 \div 50 = 0.24 \text{ W}$	✓
	Maximum power transfer occurs when $R = 23 \Omega$.	
		30 marks

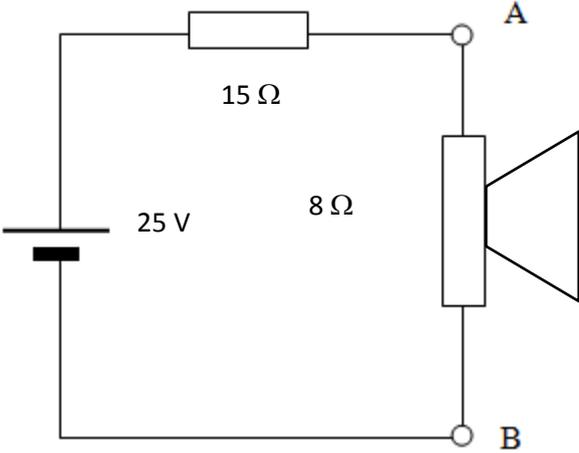2.	<p>The diagram shows an amplifier that is modelled using Thévenin's theorem.</p>  <p>The output voltage is 25 V and the loudspeaker has an impedance of 8 ohms. The internal impedance of the amplifier is 15 ohms.</p>	
(a)	Explain why the term impedance is used instead of resistance.	(3)
	Alternating signals are used.	✓
	There are reactive components within the amplifier and loudspeaker...	✓
	...for example inductance in the loudspeaker.	✓
	In this question we are going to model the circuit as a DC source of potential difference 25 V and of internal resistance 15 ohms driving a load of 8 ohms	
(b)	Show that the current in the circuit is about 1.1 A.	(2)
	$R + r = 15 + 8 = 23 \text{ ohms}$	✓
	$I = 25 \text{ V} \div 23 \Omega = 1.09 \text{ A} (\approx 1.1 \text{ A})$	✓
(c)	Calculate the power given out by the speaker.	(2)
	$P = 1.087^2 \times 8$	✓
	$P = 9.45 \text{ W}$	✓



	(d)	Calculate the total power given out by the source		(2)
		$P = 25 \times 1.087$		✓
		$P = 27.2 \text{ W}$		✓
	(e)	Work out the efficiency of the amplifier when driving an 8 ohm load.		(2)
		$\text{Efficiency} = (9.45 \div 27.2) \times 100 \%$		✓
		$\text{Efficiency} = 35 \%$		✓
	(f)	Theory tells us that the maximum power transfer occurs when the internal resistance and the load resistance are both equal. This can be achieved by the use of a load-matching transformer. What should the resistance of the primary and secondary be to achieve this?	4.6	(2)
		Primary: 15Ω		✓
		Secondary: 8Ω		✓
	(g)	Work out the turns ratio for the matching transformer	4.6	(2)
		$\text{Ratio} = (15 \div 8)^{0.5}$		✓
		$\text{Ratio} = 1.37:1$		✓
	(h)	The output transformer has a primary of 2000 turns. What is the number of turns on the secondary?	4.6	(2)
		$\text{Secondary turns} = 2000 \div 1.37$		✓
		$\text{Secondary turns} = 1460$		✓
	(i)	Show that the power transferred to the loudspeaker is now about 10 W. State what assumption you have made.	4.6	(4)
		Total resistance is now 30 ohms		✓
		$\text{Current} = 25 \div 30 = 0.833 \text{ A}$		✓
		$\text{Power} = 0.833^2 \times 15 = 10.4 \text{ W} (\approx 10 \text{ W})$		✓
		Assuming that there are no losses in the transformer.		✓
				<i>21 marks</i>

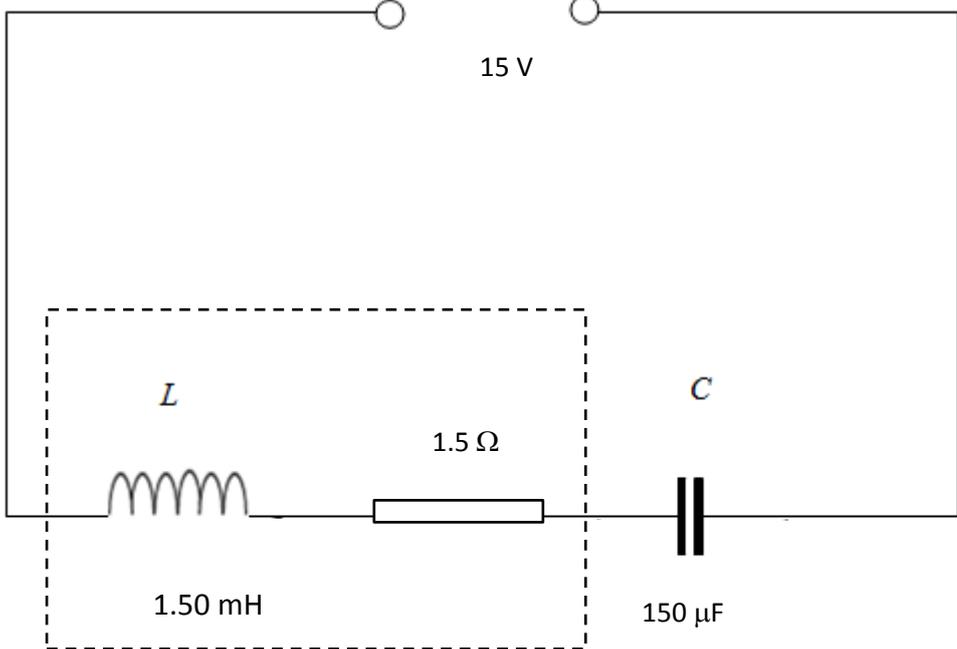3	<p>An inductor of inductance 150 mH and of resistance 1.5 Ω is placed in series with a capacitor of 150 μF, as shown in this diagram:</p> 		
	(a) How do you model an inductor with a known resistance?	(2)	
	A perfect inductor...		✓
	... in series with a resistor.		✓
	(b) Show that the resonant frequency for this combination is about 340 Hz	(2)	
	$f = 1 \div (2 \times \pi \times (1.50 \times 10^{-3} \times 150 \times 10^{-6})^{0.5})$		✓
	$f = 1 \div (2 \times \pi \times (2.25 \times 10^{-6})^{0.5})$		
	$f = 336 \text{ Hz } (\approx 340 \text{ Hz})$		✓
	(c) Calculate the reactance of the inductor at resonance frequency. Give your answer to an appropriate number of significant figures.	(3)	
	$X_L = 2 \times \pi \times 336 \times 1.50 \times 10^{-3}$		✓
	$X_L = 3.16 \Omega$		✓
	Answer to 3 significant figures as data are to 3 s.f.		✓
	(d) Write down the definition of the Q factor	5.4 (1)	
	The ratio between the inductor voltage and the supply voltage		✓

	(e)	Work out the Q factor for this circuit	5.4	(2)
		$Q = (2 \times \pi \times 336 \times 1.50 \times 10^{-3}) \div 1.50$		✓
		$Q = 2.1$		✓
	(d)	What is the voltage across the inductor?	5.4	(2)
		$V_L = 2.11 \times 15$		✓
		$V_L = 31.7 \text{ V}$		✓
				<i>12 marks</i>


4.	The circuit below is used to investigate parallel resonance:		
(a)	Show that the resonant frequency of this circuit is about 2700 Hz. (Use the “exact” formula.)	6.4	(3)
	$f_0^2 = (1/4 \pi^2) \times ((1.5 \times 10^{-3} \times 2.2 \times 10^{-6})^{-1} - (5^2 \div (1.5 \times 10^{-3})^2))$		✓
	$f_0^2 = (1/4 \pi^2) \times ((303 \times 10^6) - (11.1 \times 10^6))$		
	$f_0^2 = (1/4 \pi^2) \times (292 \times 10^6)$		✓
	$f_0^2 = 7.40 \times 10^6$		
	$f_0 = 2720 \text{ Hz}$		✓
(b)	<p>A student looks at the formula you used to calculate your answer above, and decides to use the simpler formula below instead to work out the resonant frequency:</p> $f = \frac{1}{2\pi\sqrt{LC}}$ <p>(i) What is the resonant frequency given by this formula? (ii) Under what circumstance is the use of this formula justified? (iii) What is the percentage error in the approximation?</p>	6.4	(5)
	(i) $f_0 = (2 \times \pi \times (1.5 \times 10^{-3} \times 2.2 \times 10^{-6})^{0.5})^{-1}$		✓
	$f_0 = 2770 \text{ Hz}$		✓
	(ii) When R is small (compared to the reactances)		✓
	(iii) The result is 50 ohms too large.		✓
	This represents an error of $(50 \div 2720) \times 100 = 1.84 \%$		✓

	(c)	Explain what happens when there is resonance and explain how the circuit above can act as a stable frequency source.	6.6	(4)
		At resonance, energy is exchanged...		✓
		...between the capacitor and inductor.		✓
		The impedance is very high.		✓
		So the current is very low.		✓
		The circuit gives a particular frequency...		✓
		...that is independent of voltage and current.		✓
		<i>(any 5 for 1 mark each)</i>		
	(d)	Give one other use for a resonant circuit.		(1)
		Radio receiver OR Electrical filter.		✓
				<i>13 marks</i>

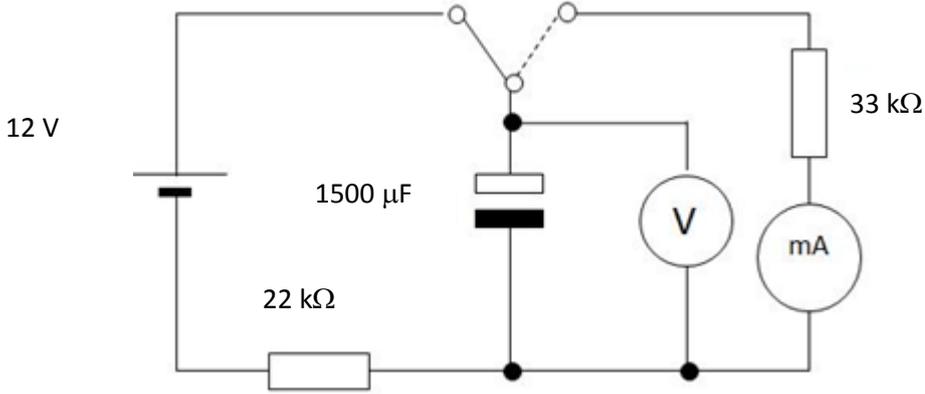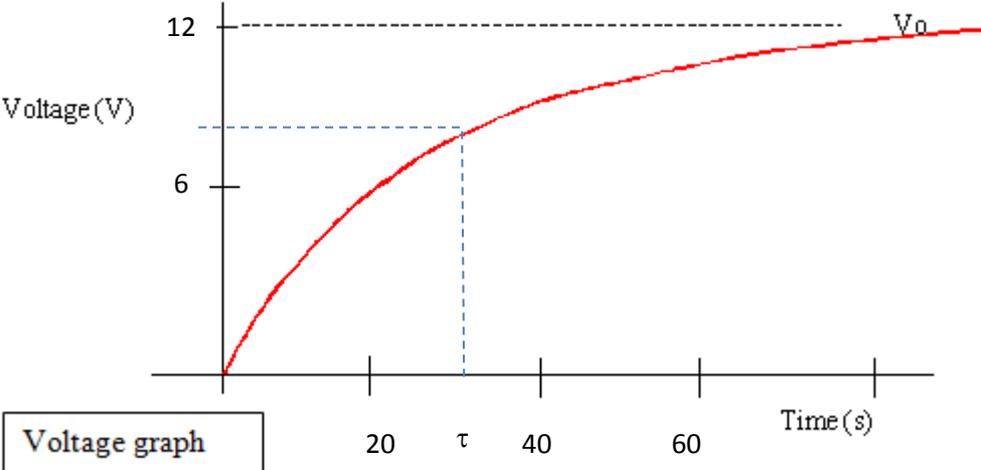5.	<p>The circuit below is being used to show the exponential charge or discharge of a capacitor through a resistor connected to a d.c. supply. The circuit as shown represents the charging of the capacitor.</p> 		
(a)	One reading you can take for both charging and discharging is time (which you do with a stopwatch). What one other reading can you take while the capacitor is charging?	8.1	(1)
The voltage			✓
(b)	Explain why reactance is not a relevant quantity in this question.	8.1	(1)
The capacitor is connected to a DC supply.			✓
(c)	Define the time constant for the charge of the capacitor. Work out the time constant.	8.3	(3)
Time taken for the voltage to reach 63 % of the final voltage			✓
$\tau = 22\,000 \times 1500 \times 10^{-6}$			✓
$\tau = 33\text{ s}$			✓
(d)	Sketch the graph of voltage against time for the charge of the capacitor. Put suitable values on your sketch graph. Mark on the time constant.	8.2	(3)
			✓ ✓ ✓


6.	A circuit consists of a pure inductor that is connected in series with a resistor as shown below.		
	Voltage is measured across the 2.0 Ω resistor. Switch S is closed.		
	(a)	Why is a data logger used?	8.5 (1)
	The time for the rise in voltage is very short.		✓
	(a)	Calculate the energy held in the inductor while the current is flowing through it.	8.5 (3)
	$I = 12 \div 2 = 6 \text{ A}$		✓
	$E = \frac{1}{2} \times 150 \times 10^{-3} \times 6^2$		✓
	$E = 2.7 \text{ J}$		✓
	(b)	When switch S is opened, the current falls to zero in 10 ms. Work out the EMF induced when switch S is opened.	8.7 (2)
	$E = (-) 0.150 \times (6 \div (-)1 \times 10^{-2})$		✓
	$E = 90 \text{ V (enough to give you a tingle)}$		✓
	(c)	Switch S is closed again. The voltage across the 2.0 ohm resistor is measured using a fast data-logger. An inductive rise is observed. Sketch a graph of the voltage against time that you would expect to see. No values are needed. Explain why it is this shape.	8.5 8.6 (4)
			✓ ✓

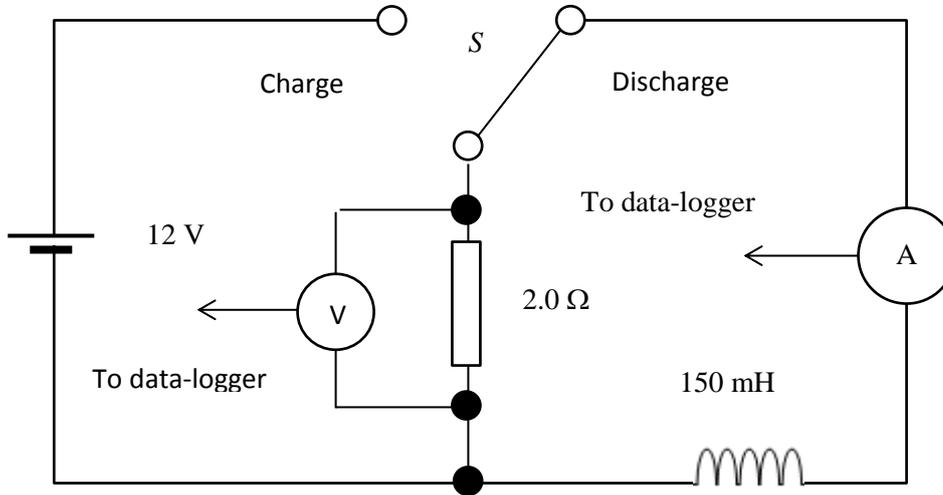A student tried to investigate the exponential fall of voltage in an inductive circuit by using the circuit in Question 6. The reverse voltage spike that you worked out in 6 (b) was sufficient to ruin the voltage sensor. So he set up a different circuit:



The components are the same as in Question 6. The time constant is 75 ms.

7.			
(a)	Suggest why this circuit should work better than the one in Question 6 when it's disconnected from the supply	8.5	(3)
	The inductor will discharge...		✓
	...through the resistor.		✓
	The maximum voltage is 12 V.		✓
(b)	Work out the time taken for the voltage to fall from 12.0 V to 6.0 V when switch S is moved to the discharge position.	8.7	(3)
	$6 = 12 \times e^{(-t/0.075)}$		✓
	$\ln 0.5 = -t \div 0.075$		✓
	$t = 52 \text{ ms}$		✓

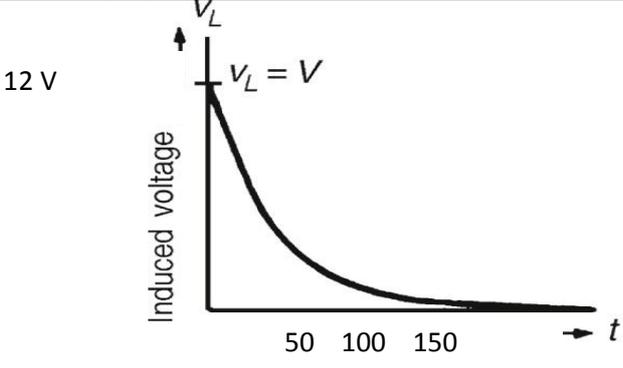	(c) In the space below, sketch the voltage-time graph from when the switch is moved to the discharge position. Put appropriate values on your sketch graph.	8.6	(3)	
				
				✓
				✓
			✓	
			<i>9 marks</i>	
			<i>Total = 120 marks</i>	

End of Examination
Now go back and check your work