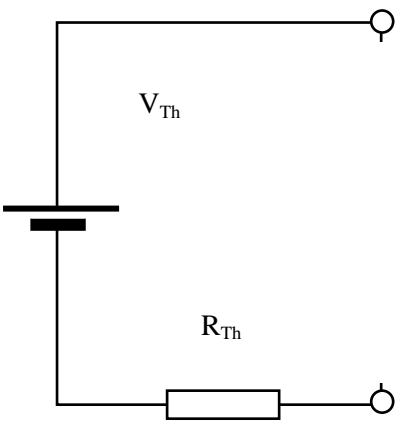
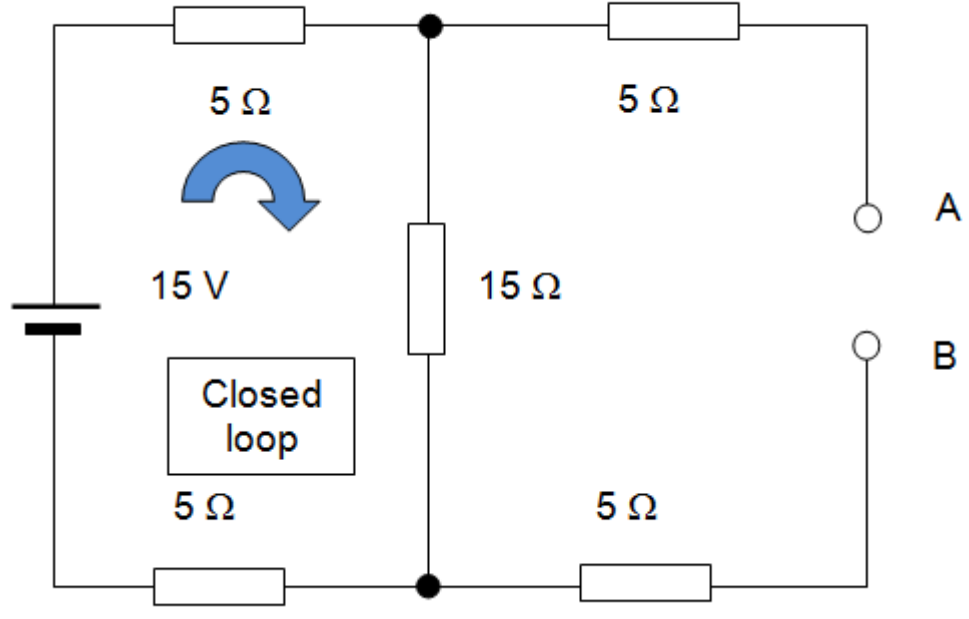


Self Test Answers

| | | | | |
|----|-----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------|-----|
| 1. | (a) | Leon Thévenin proposed a rule that enabled electrical engineers to simplify complex power supplies. In the space below, write down the rule and draw a circuit that shows the rule | 4.4 | (3) |
| | | All circuits, however complex... |  | |
| | | ... can be treated as: | | |
| | | ... a simple perfect battery... | | ✓ |
| | | ... in series with a resistor. | | ✓ |
| | | | | |
| | | | | ✓ |
| | (b) | <p>The circuit below is being used as a source of voltage.</p>  | 4.4 | |
| | (i) | Show that the Thévenin voltage across AB is 9 V | 4.4 | (2) |
| | | R_T in closed loop = $5 + 15 + 5 = 25$ ohms | | ✓ |
| | | $V_{Th} = (15 \div 25) \times 15$ | | |
| | | $V_{Th} = 0.6 \times 15 = 9$ V (QED) | | ✓ |

| | | | | |
|--|------|---------------------------------------------------------|-----|-----|
| | (ii) | Calculate the Thévenin resistance. | 4.4 | (3) |
| | | $R^{-1} = 10^{-1} + 15^{-1} = 0.167$ | | ✓ |
| | | $R = 0.167^{-1} = 6 \text{ ohms}$ | | ✓ |
| | | $R_{Th} = 5 + 6 + 5 = 16 \Omega$ | | ✓ |
| | | | | |
| | (c) | A 10 ohm resistor is now placed across the gap AB. | 4.4 | |
| | (i) | Calculate the current across the 10 ohm resistor. | | (2) |
| | | $R = 10 + 16 = 26 \text{ ohms}$ | | ✓ |
| | | $I = 9 \div 26 = 0.35 \text{ A}$ | | ✓ |
| | | | | |
| | (ii) | Calculate the voltage across the 10 ohm resistance. | | (2) |
| | | $V = IR = 0.35 \times 10$ | | ✓ |
| | | $I = 3.5 \text{ V}$ | | ✓ |
| | | | | |
| | (d) | How is Norton's theorem used to model a complex source? | | (2) |
| | | Norton sources are constant current sources... | | ✓ |
| | | ...in parallel with a resistor. | | ✓ |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |