

Electronics Unit 2 Test 4 (Answers)

Name	
Number	

You have addressed the skills being assessed in this Test.

Recognise the op-amp as a voltage comparator.	
Recognise the op-amp as an inverting amplifier.	
Explain the properties of the inverting amplifier.	
Explain the concept of virtual earth.	
Calculate the gain of an inverting amplifier.	
Recognise the non-inverting amplifier.	
Calculate the gain of a non-inverting amplifier.	
Compare the input resistance of the inverting and non-inverting amplifier.	

There are things that you need to do to improve your work:



Ensure that you use good English...	
...and clear presentation.	
Correct use of technical terms.	
Not to leave questions un-attempted.	
Show your working out fully.	
Include units as part of your final answer	


<p>Comment:</p>

<p>Mark: ____ / 45</p> <p>Grade: _____</p> <p>MTG: _____</p>
--

1.	The circuit below shows a simple thermostat circuit to control temperature in a greenhouse	
(a)	Complete the sentence:	1
	The op-amp is being used as a <u>voltage comparator</u>	✓
(b)	In the space below draw a system diagram for the circuit. One box has been completed as an example.	5
(c)	Complete the circuit diagram by adding a component that will protect the MOSFET.	3
(d)	Explain why the component you have just added is needed.	2
	Relay is an electromagnetic device	✓
	Gives a high reverse voltage spike when turned off	✓
	This can wreck the MOSFET.	✓

	(e)	At a certain temperature the resistance of the thermistor is 7.0 kilohms. Calculate the voltage at the inverting input.	2
		$V_{out} = 12(4700 \div (7000 + 4700))$	✓
		$V_{out} = 4.8 \text{ V}$	✓
	(f)	What is the voltage at the non-inverting input? Explain your answer.	2
		4.8 V	
		The difference between the inputs is very small.	
	(g)	When the greenhouse is cold, explain how the heater comes on.	3
		The resistance of the thermistor is high	✓
		The output of the voltage divider circuit is low	✓
		Voltage of the inverting input is lower than the non-inverting input	✓
		Op amp gives out a high (positive) voltage (to turn on the MOSFET).	✓
	(h)	When the greenhouse is warm, explain how the heater remains switched off	2
		The resistance of the thermistor is low	
		The output of the voltage divider circuit is high	
		Voltage of the inverting input is higher than the non-inverting input	
		Op amp gives out a negative voltage	
		The MOSFET remains turned off.	

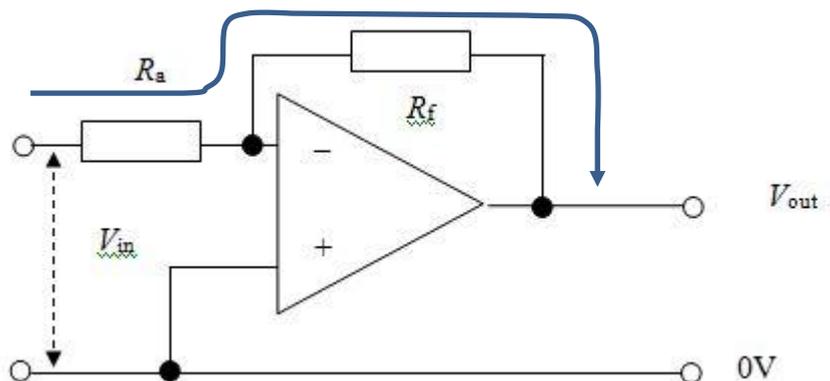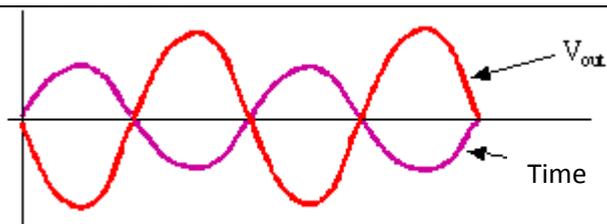2.	<p>The diagram shows an operational amplifier used in inverting mode</p> 	
(a)	On the diagram, draw a line to show where the current flows.	2
(b)	State what assumption you made, giving a reason	2
	No current goes into the op-amp...	✓
	...because the resistance is extremely high.	✓
(c)	Explain what is meant by a <i>virtual earth</i> .	2
	The inverting input is almost at 0 V...	
	...because the voltage difference is very small.	
(d)	The amplifier has $R_a = 2.2 \text{ k}$ and $R_f = 820 \text{ k}$. If the input voltage = 6 mV, calculate the output voltage.	3
	$V_{out}/V_{in} = -820 \div 2.2 = -370$	✓
	$V_{out} = -2.24 \text{ V}$	✓
		✓
(e)	The amplifier has a unity gain bandwidth constant of 125 000. What is the bandwidth?	2
	Bandwidth = $125\,000 \div 370$	
	Bandwidth = 338 Hz	
(f)	In the space below, sketch the sinusoidal input waves and the output waves to show the phase difference.	2
	<p>Voltage</p>  <p>Time</p>	<p>✓</p> <p>✓</p>

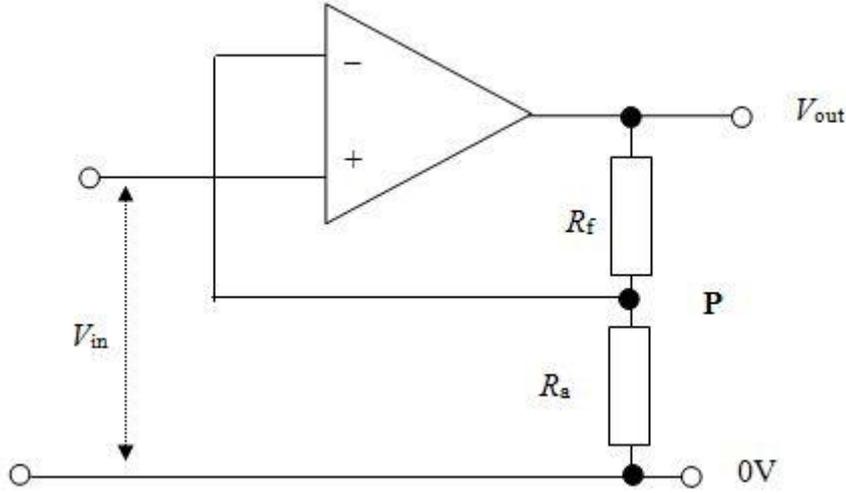3.	<p>The circuit diagram shows a non-inverting amplifier.</p> 	
(a)	Explain why this circuit uses negative feedback.	2
	Feedback loop is fed into...	✓
	...the inverting input.	✓
(b)	Calculate the voltage gain if $R_a = 33\text{ k}$ and $R_f = 270\text{ k}$.	2
	$\text{Gain} = 1 + R_f/R_a = 1 + (270 \div 33)$	✓
	Gain = 9.18	✓
(c)	A 100 k resistor is placed in series with the non-inverting input. Explain what difference, if any, will be made to the gain of the amplifier.	3
	No difference	✓
	Input resistance to non-inverting input...	✓
	...is much higher than 100 k .	✓
(d)	With reference to the input resistance and phase, explain the advantage of using a non-inverting amplifier to an inverting amplifier.	4
	The non-inverting amplifier has an almost infinite input resistance...	✓
	...while the input resistance of the inverting op-amp is R_a .	✓
	The input and output of the non-inverting op-amp are in phase...	✓
	...while those of the inverting op-amp are 180° out of phase.	✓
Total = 45 marks		

End of Examination.

Now go back and check your work.